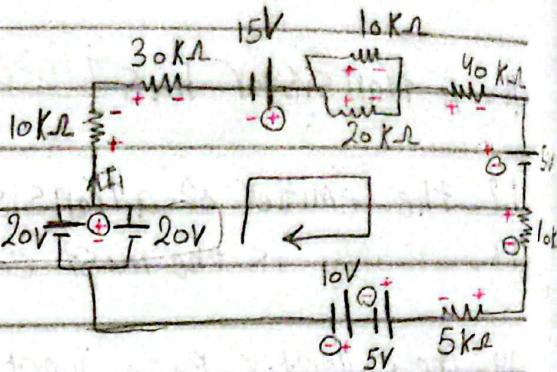


Subject _____

Date / /

1 - Total Voltage = _____



$$V_T = 20 + 15 - 5 - 5 - 10 = 15V$$

2 - Total Resistance = _____

$$R_T = 10 + 30 + \frac{10 \times 20}{10+20} + 40 + 10 + 5 = 101.67\text{ k}\Omega$$

3 - Total Current = _____

$$I = \frac{V}{R} = \frac{15}{101.67 \times 10^3} = 147.5 \times 10^{-6} = 148\text{ }\mu\text{A}$$

4 - Current in R_2 = _____

$$IR_2 = 148\text{ }\mu\text{A}$$

$$V = IR$$

5 - Which of the following statements doesn't represent ohm's law?

a) Current/Potential difference = constant $\rightarrow \frac{I}{V} = \frac{1}{R} \rightarrow V = IR$ ✓

b) Potential difference/Current = constant $\rightarrow \frac{V}{I} = R \rightarrow V = IR$ ✓

c) Potential difference = Current \times Resistance $\rightarrow V = I \times R$ ✓

d) Current = resistance \times Potential difference INSULATOR $\rightarrow I = R \times V$ ✗

✓ 6 - Kirchhoff's voltage law is based on law of conservation of energy

✓ 7 - Diode has one depletion region.

✓ 8 - The most widely used rectifier is bridge full wave rectifier.

✓ 9 - Diode characteristic curve is plot between Voltage & Current.

✓ 10 - Smoothing circuit used in amplifiers True.

KAMS

11. A transistor has three terminals. ✓
12. the emitter of a transistor is heavily doped. ✓
13. Silicon is the most commonly semiconductor to manufacture a transistor.
14. The collector-base junction in a transistor has reverse bias at all times.
15. majority carriers in N-type semiconductor are electrons.
15. majority carriers in P-semiconductor are holes. ✓
16. in PNP semiconductor, the base is N-semiconductor. ✓
17. Bridge full-wave rectifier used to convert AC signals to DC signals.
- ✓ 18. the important mode of transistor is all of the above
 → active mode
 → cut off mode
 → saturation mode
19. Transistor as amplifier can be all of the above. ✓
20. Symbol of transistor none of the above.
21. The op-amp can amplify both AC and DC signals.
22. A differential amplifier is a part of an op-amp.
23. An ideal operational amplifier has infinite bandwidth.
24. An operational amplifier contains a differential amplifier, a voltage amplifier, and an output amplifier. TRUE
25. The inverting input is Pin 3. TRUE
26. The ideal output impedance for an operational amplifier is infinite. TRUE
27. Two resistors of 100Ω and 200Ω are connected in parallel. The overall resistance will be - 0Ω -.
28. The capacitance C depends on All of the above
 → the dielectric constant of the material between the plates.
 → the area of a plate.
 → the distance between plates.
29. The unit of inductance is Henry.
30. in a pure inductive circuit the current lags behind the voltage by 90° .
31. Equivalent circuit laws for inductors in series and parallel is similar to that for resistors to that for resistors.

ANS

Subject _____

Date / /

32. In p-type extrinsic semiconductors, defect are located above valence band. ✓

✓ 33. Output Voltage can be limited bigger than 0.7 by diode limiter.
33. Output Voltage can be limited bigger than 0.7 by diode limiter
34. Silicon controlled rectifier can be controlled by the gate.

✓ 35. The β of the transistor is the ratio of I_C and I_B True

36. A Semiconductor is formed by None of the above bonds.

Co-ordinate Ionic Electrovalent

37. The input control parameter of a JFET is - - -

38. A crystal diode utilises forward-reverse characteristic for rectification.

39. The current across a PN junction is due to minority carriers.

40. A MOSFET has Four terminals

Date / /
Subject _____

1- Using a circuit, find the current in R_S


$$\Sigma V = 0$$

$$L = -20 + (10 \times 10^3) I_1 + (30 \times 10^3) I_1 + (4 \times 10^3) I_1 - 15$$

$$(40 \times 10^3) I_1 + 5 + (10 \times 10^3) I_1 + (5 \times 10^3) I_1 + 5 + 10$$

$$= 0$$
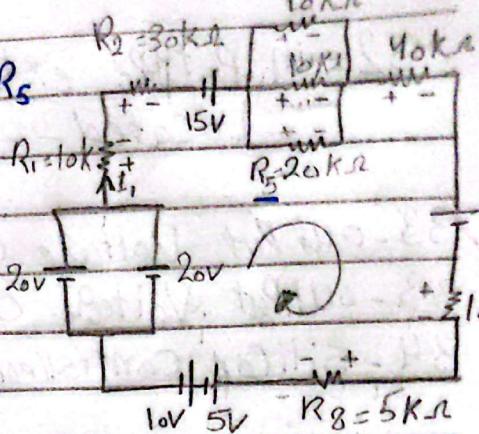
$$-15 + (99 \times 10^3) = 0 \rightarrow I_1 = 1.5 \times 10^{-4} A$$




$$V = IR = 1.5 \times 10^{-4} \times 4 \times 10^3 = .6 V$$

$$I = \frac{V}{R} = \frac{.6}{20 \times 10^3} = 3 \times 10^{-5} A$$

$$2- I_4 = 20 \times 10^{-3} - 5 \times 10^{-3} = 25 \times 10^{-3}$$

$$I_4 = -10 \times 10^{-3} A$$
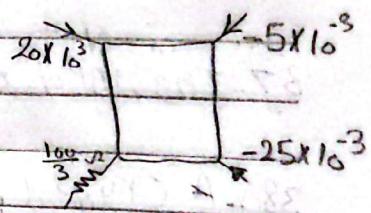
$$V = IR = 10 \times 10^{-3} \times \frac{100}{3} = \frac{1000}{3} V$$



3- How transistor can be used as amplifier and in which mode:

① Common Base


1. Emitter is input side and collector is output side.

2. Base is between input and output side.

3. Collector connected to Base reverse.

4. Emitter connected to Base forward.

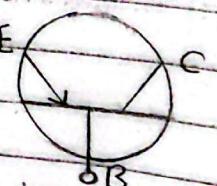5. $I_E = I_C + I_B$ $\because I_C \approx I_E$ \rightarrow because I_B is small
 $I_C = \alpha I_E \rightarrow \alpha = \frac{I_C}{I_E}$



② Common Emitter

1. We connected input signal between Base and Emitter.
 2. We connected output signal between Emitter and collector.



③ Common Collector

1. We connected input signal between Collector and Base.
 2. We connected output signal between Collector and Emitter.




4- How does Field effect transistor (FET) work?

1-Basic Structure:

- **SOURCE(S)**: The terminal where current enters the channel.
- **DRain(D)**: The terminal where current exits the channel.
- **GATE(G)**: the terminal that controls the current flowing through the channel.

2-types of FETs:

FET

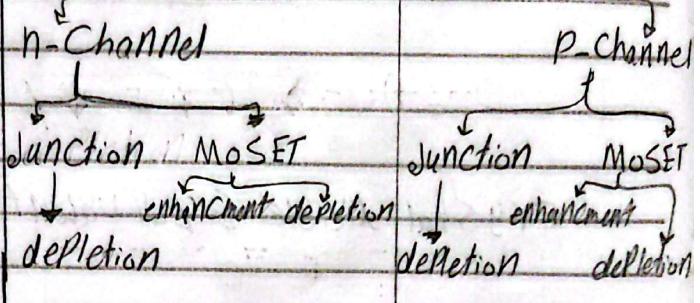



3- Current Control:

N-Channel:

positive Voltage on gate \rightarrow Electrons Flow \rightarrow Current goes from Source to drain.

P-Channel:

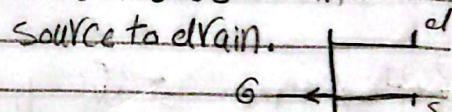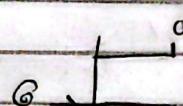
Negative Voltage on gate \rightarrow holes flow \rightarrow current goes from source to drain.



✓ 5 - what is the operational amplifier? Giving 8 applications of it.


Operational amplifier: is an operation to amplify the weak signal.

Linear/simple (inverting)

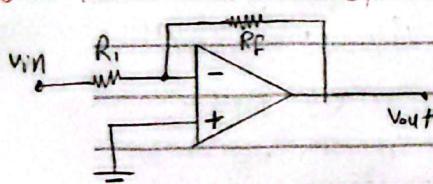


$$V_{out} = -\frac{R_f}{R_i} V_{in}$$

adder (inverting)

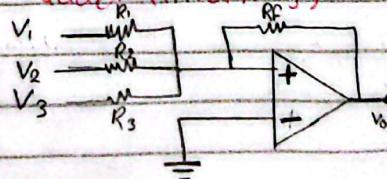


$$V_{out} = \left(\frac{R_f V_1}{R_1} + \frac{R_f V_2}{R_2} + \frac{R_f V_3}{R_3} \right)$$

integrator (inverting)

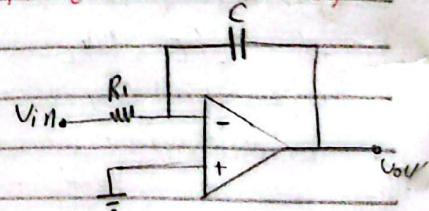


$$V_{out} = -\frac{1}{Rc} \int V_{in} dt$$

buffer (inverting)

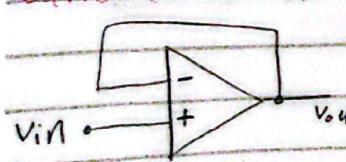


IAMS

substractor (inverting)

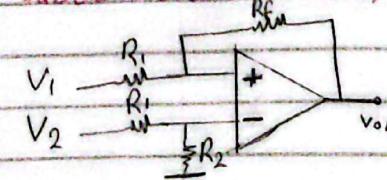

$$V_{out} = \frac{R_f}{R_1} (V_2 - V_1)$$

differentiator (inverting)

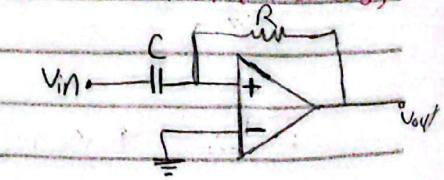


$$V_{out} = RC \frac{dV_1}{dt}$$

b- Write short note about: ✓✓

a - Microscopic model of current:

A Current: the amount of charge that run into the tube in one second.
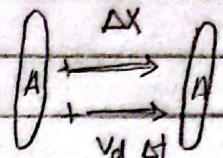
$$I = \frac{Q}{t} = n \cdot A \cdot \frac{q}{\Delta x} = n \cdot A \cdot \frac{q}{E} = n \cdot A \cdot V_d \cdot q$$




b- Crystal diode Equivalent Circuits: ✓✓✓

model

draw



short note

ideal Model

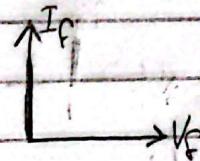


act close(on) and open(off) switch

Simplified Model

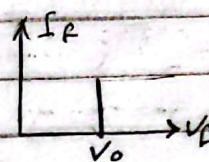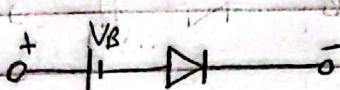

ideal model and V called barrier Potential = 0.7V

Approximate Model

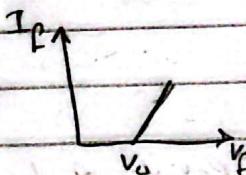

simplified model and a small dynamic resistance

c- Extrinsic Semiconductors: semiconductor has been doped with: ✓✓

1) Pentavalent (Valency 5)

n-type → like: As, Sb, P

→ majority carriers: electrons



→ minority carriers: holes

2) Trivalent (Valency 3)

p-type → like: In, B, Al

→ majority carriers: holes

→ minority carriers: electrons

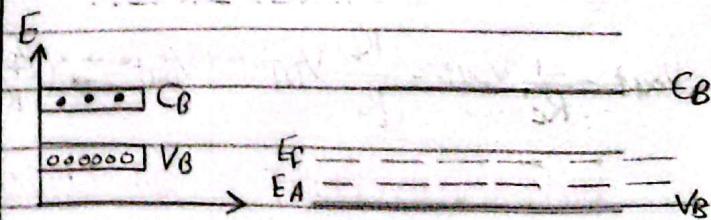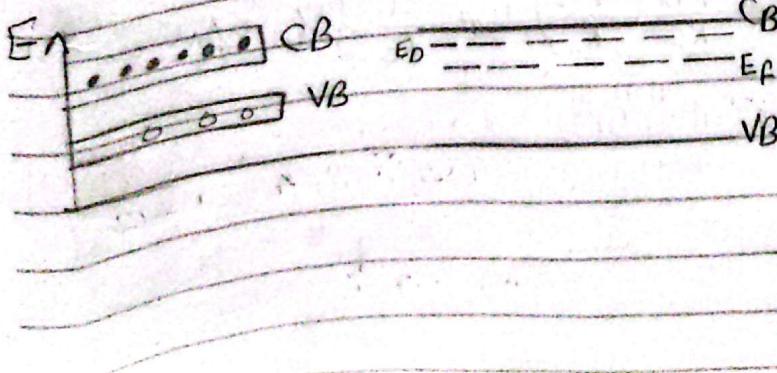


d- Voltage limiter: this device can be limited to a specific value, it should not exceed $\pm 0.3V$

if we want to change this limit \rightarrow adding a battery



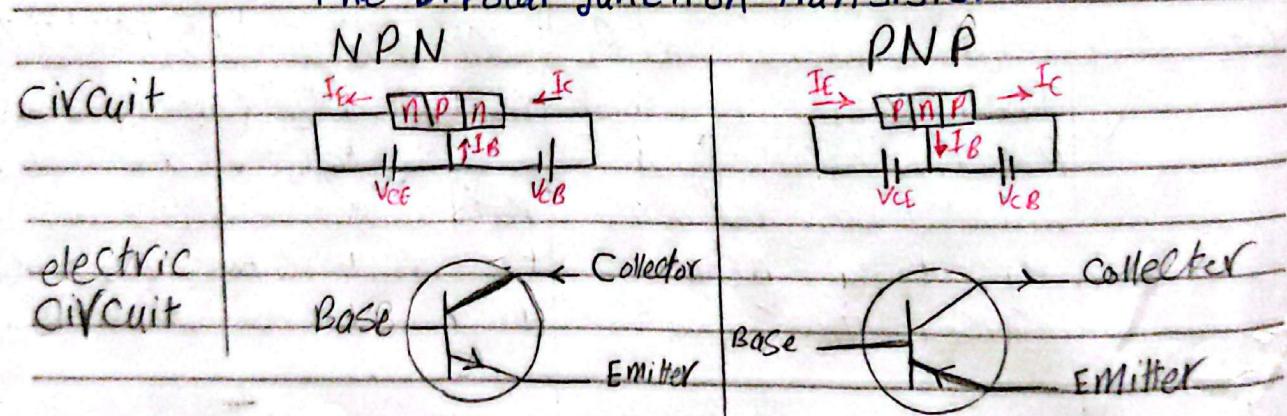7- Compare between the modes and the configurations of the Bipolar junction transistor



8- Find the current flowing in the circuit:

$$\text{in (a) Point} \rightarrow \sum I = 0$$

$$\rightarrow I_1 - I_2 - I_3 = 0 \quad ①$$

in loop (1):


$$-45 + 0.5I_3 + 1.5I_3 + 6I_1 = 0$$

$$\rightarrow 6I_1 + 0I_2 + 2I_3 = 45 \quad ②$$

in loop (2):

$$2.5I_2 - 18 + 0.5I_2 + 6I_1 = 0$$
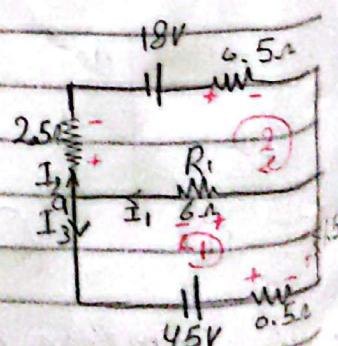
$$\rightarrow 6I_1 + 3I_2 + 0I_3 = 18 \quad ③$$




①, ②, ③ with calculator

$$I_1 = 4.75 \text{ A} \quad I_2 = -3.5 \text{ A}$$

$$I_3 = 8.25 \text{ A}$$

KMS

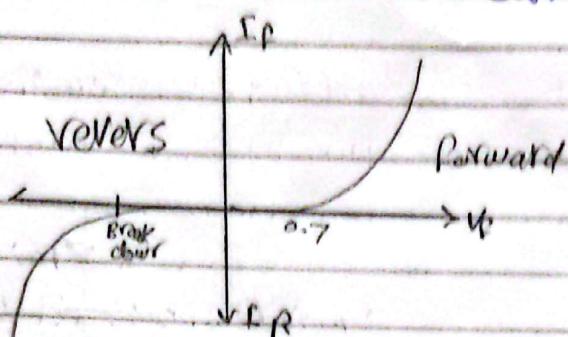g- Write short note about:
b- diode characteristic curve:



C- Rectifiers:



Half wave rectifier

Note short Contain a diode and R_L
The current is pass to half positive because it is a forward bias and don't pass to half negative because it is reverse bias.

Full wave rectifier

contain a two diode and R_L resistance. The current is pass a D_1 to positive direction not pass a negative direction. the current is pass a D_2 to negative direction not pass a positive direction.

draw

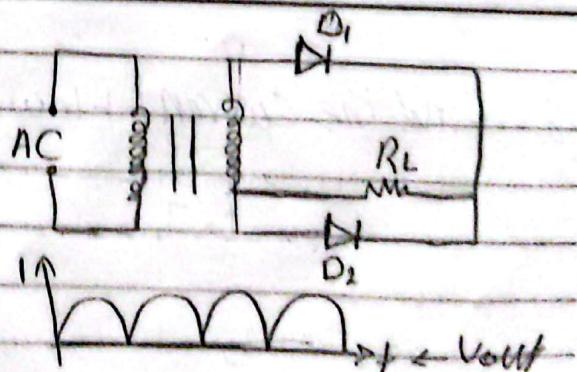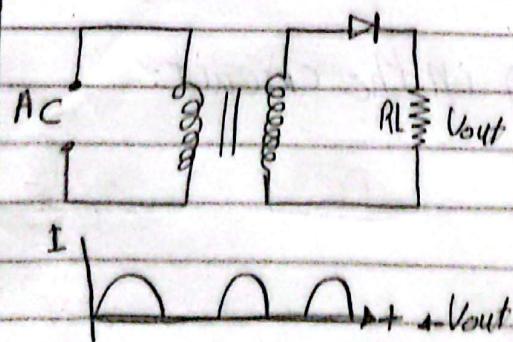

10. Compare between the biPolar Junction transistor and Field effect Transistor

BJT \rightarrow 7 pages

FET \rightarrow 4 pages

Kous

Subject _____

Date / /

II- Compare between intrinsic and extrinsic semiconductor:

	Intrinsic semiconductor	Extrinsic semiconductor
Carriers	Holes & electrons	N-type \rightarrow electrons P-type \rightarrow holes
Number of electrons and holes	equal	N-type \rightarrow electrons $>$ holes P-type \rightarrow electrons $<$ holes
Impurities	hasn't	N-type \rightarrow Pentavalent P-type \rightarrow trivalent
Example	Si & Ge	N-type, P-type

12- find the current in the following circuit

$$\text{in (C) Point: } \Sigma I = 0$$

$$I_1 + I_2 - I_3 = 0 \quad ①$$

in loop ① :

$$-14 + 4I_2 - 10 + 6I_1 = 0$$

$$6I_1 + 4I_2 + 0I_3 = 24 \quad ②$$


in loop ② :

$$-10 + 6I_1 + 2I_3 = 0$$

$$6I_1 + 0I_2 + 2I_3 = 10 \quad ③$$

$$I_1 = -0.4 \text{ A} \quad I_2 = 6.6 \text{ A}$$

$$I_3 = 6.2 \text{ A}$$

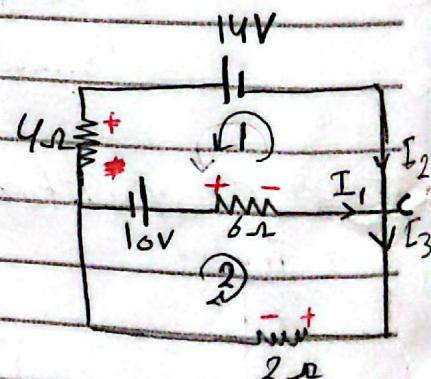

①, ②, ③ from calculator


13-(BJT) has three doped regions forming two P-N junctions between them, compare between these regions showing transistor types, characteristic curve, configurations and transistors as an amplifier.

1 different parts of a BJT

- Emitter: the region that emits charge carriers.


- Base: the middle region that controls the current flowing from the emitter to the collector.

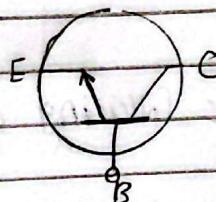- Collector: the region where charge carriers are collected after passing through the base.



2-types of Transistor:


NPN: Emitter and Collector are made of N-type, and the base is P-type.	PNP: Emitter and Collector are made of P-type, and the base is N-type.
--	--

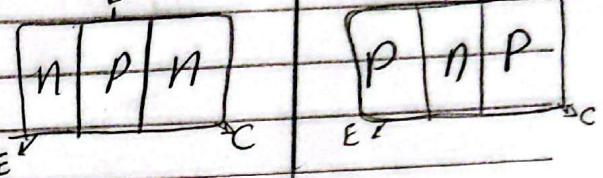

$$A_C > A_E > A_B$$

$$\alpha_E > \alpha_C > \alpha_B$$

3- characteristics curve:

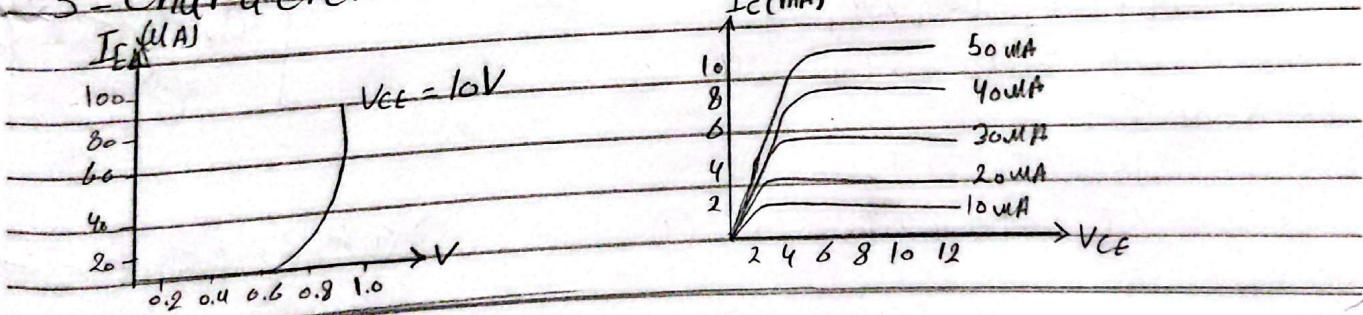


4- Configurations:

- Common Base: the Base is common between the input and output.



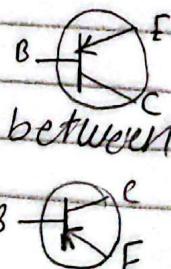- Common Collector: the Collector is common between the input and output.



- Common Emitter: the Emitter is common between the input and output.

KAMS

5-transistor as amplifier:

- It amplifies electrical signals by modulating the collector current (I_C) based on the base current I_B .


$$V_{CC} = V_{CE} + I_C R_L$$

$$\beta = \frac{I_C}{I_B}$$

Q4- Find the current in current in the flowing circuit applying Kirchhoff's laws:

From (a) Point:

$$I_0 - I_1 - I_2 = 0 \quad (1)$$

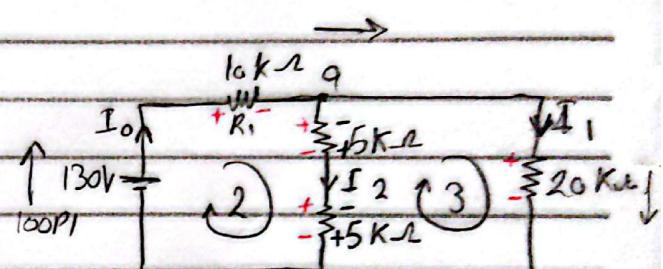

From loop 2:

$$-130 + (10 \times 10^3) I_0 + (10 \times 10^3) I_2 = 0 \quad (2)$$

From loop 3:

$$(20 \times 10^3) I_1 + (10 \times 10^3) I_2 = 0 \quad (3)$$

From calculator 1, 2, 3

$$I_0 = 4.33 \times 10^{-3} A \quad I_1 = -4.33 \times 10^{-3} A \quad I_2 = 8.6 \times 10^{-3} A$$

Habib El Nasrag

kms